


Lecture 16: Address decoding

- Introduction to address decoding
- Full address decoding
- Partial address decoding
- Implementing address decoders
- Examples




Introduction to address decoding

- **Although the memory space in the 68000 is said to be flat, it does not mean that the physical implementation of memory is homogeneous**
 - Different portions of memory are used for different purposes: RAM, ROM, I/O devices
 - Even if all the memory was of one type, we still have to implement it using multiple ICs
 - This means that for a given valid address, one and only one memory-mapped component must be accessed
- **Address decoding is the process of generating chip select (CS*) signals from the address bus for each device in the system**
- **The address bus lines are split into two sections**
 - the N most significant bits are used to generate the CS* signals for the different devices
 - the M least significant signals are passed to the devices as addresses to the different memory cells or internal registers

 

A very simple example

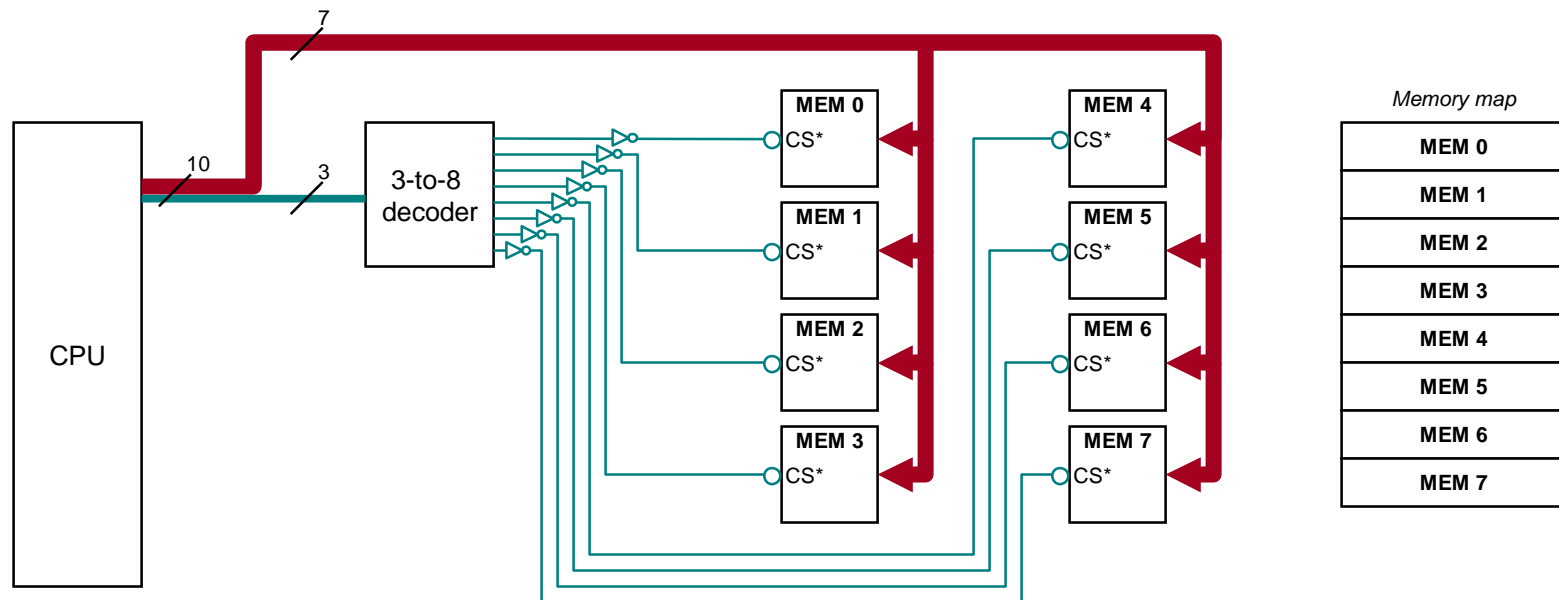- Let's assume a very simple microprocessor with 10 address lines (1KB memory)
- Let's assume we wish to implement all its memory space and we use 128x8 memory chips
- **SOLUTION**
 - We will need 8 memory chips ($8 \times 128 = 1024$)
 - We will need 3 address lines to select each one of the 8 chips
 - Each chip will need 7 address lines to address its internal memory cells



Address decoding methods

- **The previous example specified that all addressable memory space was to be implemented but**
 - There are some situations where this requirement is not necessary or affordable
- **If only a portion of the addressable space is going to be implemented there are two basic address decoding strategies**
 - Full address decoding
 - All the address lines are used to specify a memory location
 - Each physical memory location is identified by a unique address
 - Partial address decoding
 - Since not all the address space is implemented, only a subset of the address lines are needed to point to the physical memory locations
 - Each physical memory location is identified by several possible addresses (using all combinations of the address lines that were not used)




Full address decoding

■ Let's assume the same microprocessor with 10 address lines (1KB memory)

- However, this time we wish to implement only 512 bytes of memory
- We still must use 128-byte memory chips
- Physical memory must be placed on the upper half of the memory map

■ SOLUTION

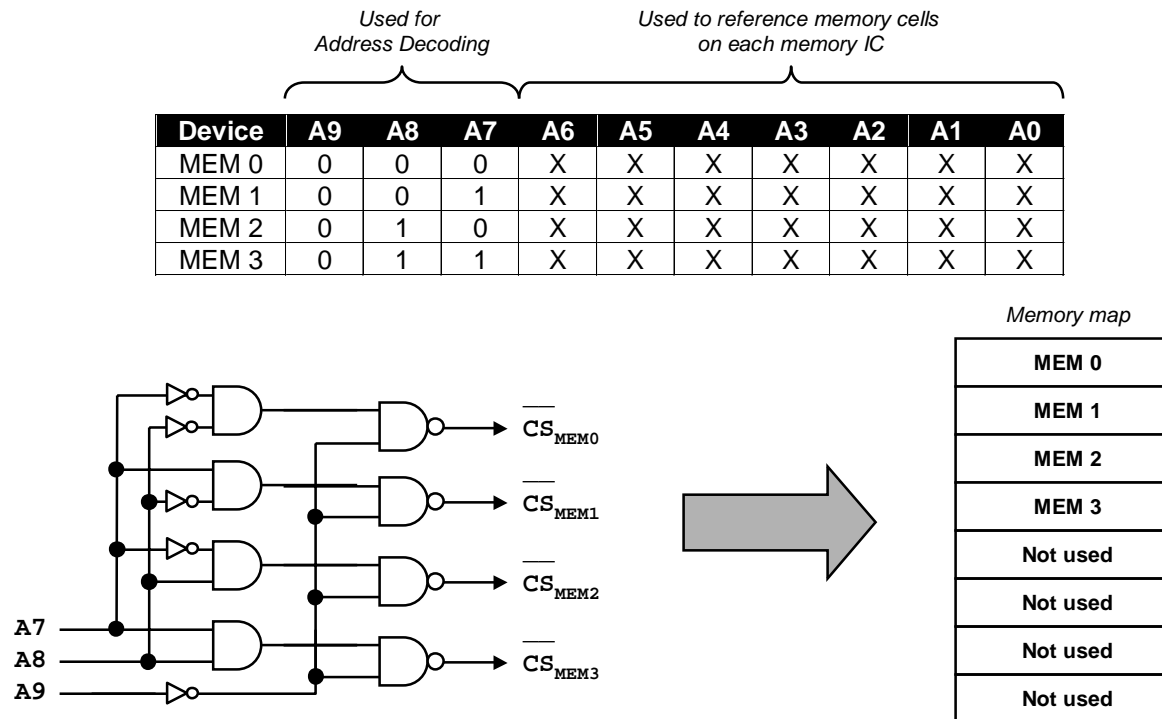



Partial address decoding

■ Let's assume the same microprocessor with 10 address lines (1KB memory)

- However, this time we wish to implement only 512 bytes of memory
- We still must use 128-byte memory chips
- Physical memory must be placed on the upper half of the memory map

■ SOLUTION

Device	Not used			Used for Address Decoding		Used to reference memory cells on each memory IC				
	A9	A8	A7	A6	A5	A4	A3	A2	A1	A0
MEM 0	X	0	0	X	X	X	X	X	X	X
MEM 1	X	0	1	X	X	X	X	X	X	X
MEM 2	X	1	0	X	X	X	X	X	X	X
MEM 3	X	1	1	X	X	X	X	X	X	X

  

Implementing address decoders

Discrete logic

- High speed (propagation signals)
- High chip-count
- Lacks flexibility

Data decoders


- More appropriate than random logic
- The selection of devices is determined by the physical wiring
- All the memory blocks must have the same size

Programmable Read Only Memory (PROM)

- Versatile, since the selection of devices is determined by the programming
- Memory blocks can be of different sizes
- Lookup tables can become very large for more than 8 address lines

Other methods (beyond the scope of the lecture) are

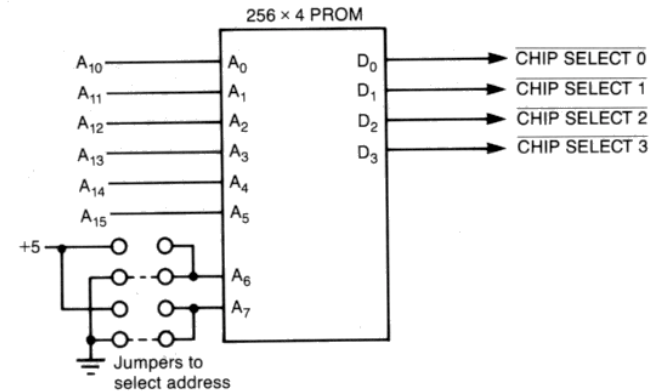- Field Programmable Gate Arrays (FPGA) and
- Programmable Address Decoders



Address	Contents	Address range	Block size
000000	1110	0000-03FF	1K
000001	1111	0400-07FF	1K, unused
000010	1101	0800-0FFF	2K
000011	1101		
000100	1011	1000-1FFF	4K
000101	1011		
000110	1011		
000111	1011		
001000	0111	2000-3FFF	8K
001001	0111		
001010	0111		
001011	0111		
001100	0111		
001101	0111		
001110	0111		
001111	0111		
010000	1111	4000-FFFF	48K, unused
.	.		
.	.		
.	.		
111111	1111		



Example 1

- A circuit containing 64K words of RAM is to be interfaced to a 68000-based system, so that the first address of RAM (the *base address*) is at \$480000

- What is the entire range of RAM addresses?
- Design a FULL address decoder using two 64K×8 RAM ICs

■ Solution


- The address range for the RAM is from \$480000 to \$480000+(128K=\$20000)=\$4A0000-1=\$49FFFF
- The two ICs must be differentiated through UDS*/LDS* (since the 68000 DOES NOT have A₀)

4				8 or 9				0 to F				0 to F				0 to F				0 to F			
A ₂₃	A ₂₂	A ₂₁	A ₂₀	A ₁₉	A ₁₈	A ₁₇	A ₁₆	A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
0	1	0	0	1	0	0	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X

These 7 address lines set the base address of the memory


These 16 address lines will select one of the 2¹⁶ (64K) locations inside each RAM IC

This address line is implemented with UDS*/LDS*

 

Example 2


- A 68000-based system is to be built with these memory requirements
 - a 16K word EPROM with a starting address of \$60 0000
 - a 16K word RAM with a starting address of \$70 0000
- Design a FULL address decoder for this application using 16K×8 chips for both EPROM and RAM
 - $\$60\ 0000 + (16\text{KWord}=32\text{KB}=\$8000)-1=\$60\ 7\text{FFF}$
 - $\$70\ 0000 + (16\text{KWord}=32\text{KB}=\$8000)-1=\$70\ 7\text{FFF}$

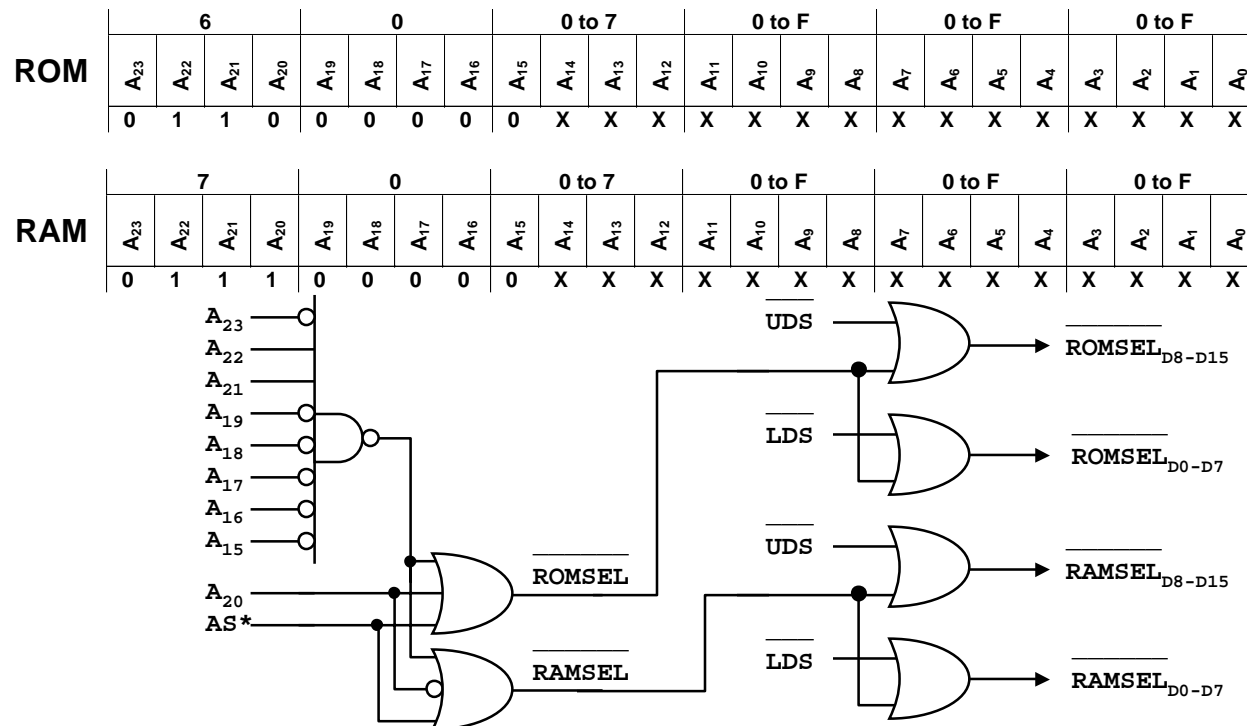

Example 3

- Design a PARTIAL address decoder for a 68000-based system with only 8K words of EPROM space, and a base address at \$4000, using 8Kx8 memory chips

0				0				4 to 7				0 to F				0 to F				0 to F			
A ₂₃	A ₂₂	A ₂₁	A ₂₀	A ₁₉	A ₁₈	A ₁₇	A ₁₆	A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	0	0	1	X	X	X	X	X	X	X	X	X	X	X	X	X	X

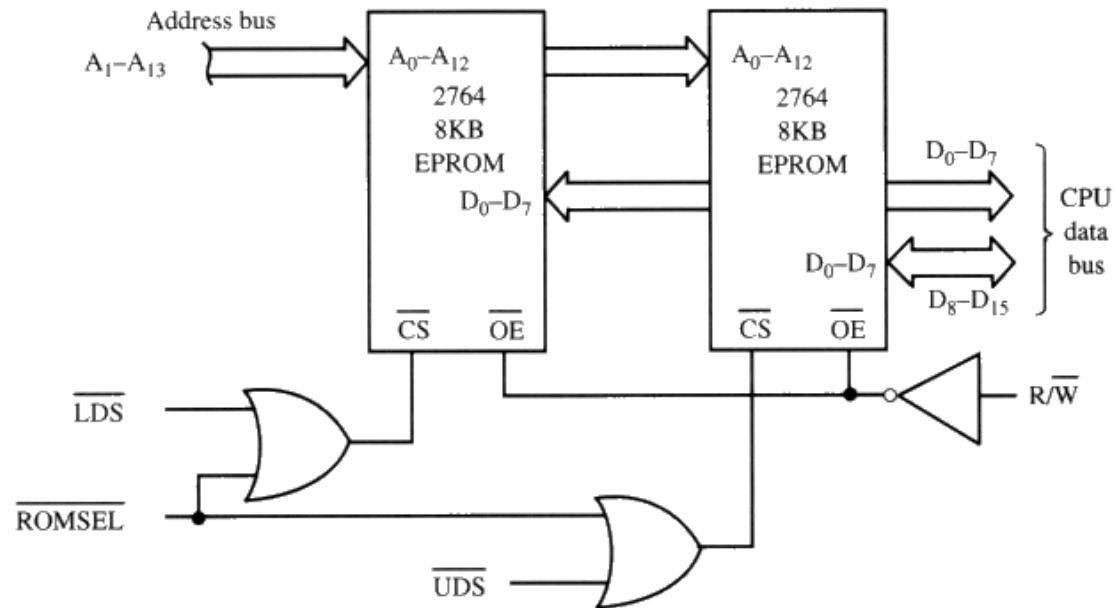


Example 4

Design a partial address decoder for a 68000-based system that contains

- 2MB of EPROM at a starting address \$00 0000 using 512Kx8 chips
- 2MB of RAM at a starting address \$10 0000 using 256Kx8 chips
- 64KB I/O space starting at \$FF0000

SOLUTION

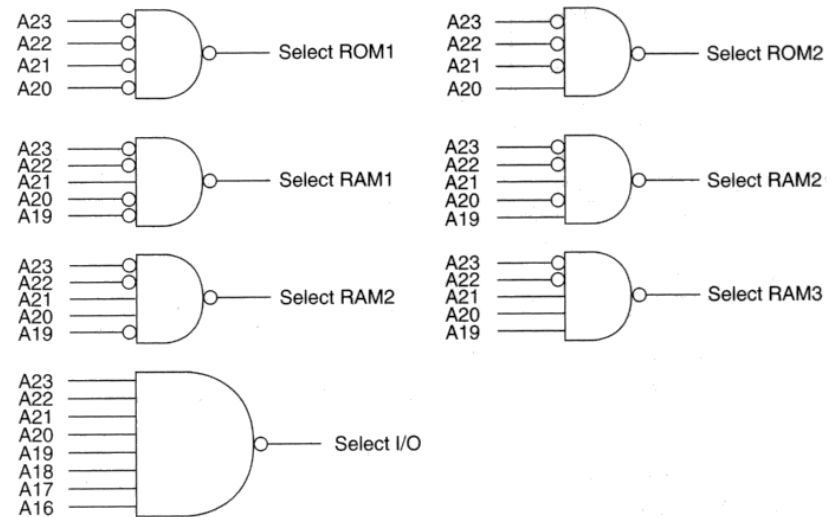- For the EPROM we will need 4 512Kx8 chips, organized as 2 pairs of 512x8 chips (in order to use UDS*/LDS*). We will call these pairs ROM1 and ROM2
- For the RAM we will need 8 256Kx8 chips, organized as 4 pairs of 256Kx8: RAM1 to RAM4



	A ₂₃	A ₂₂	A ₂₁	A ₂₀	A ₁₉	A ₁₈	A ₁₇	A ₁₆	A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₀₉	A ₀₈	A ₀₇	A ₀₆	A ₀₅	A ₀₄	A ₀₃	A ₀₂	A ₀₁	A ₀₀
ROM1	0	0	0	0	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
ROM2	0	0	0	1	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
RAM1	0	0	1	0	0	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
RAM2	0	0	1	0	1	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
RAM3	0	0	1	1	0	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
RAM4	0	0	1	1	1	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
I/O	1	1	1	1	1	1	1	1	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X

