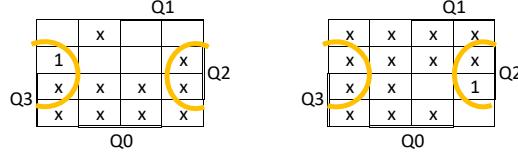


mi	Q3n	Q2n	Q1n	Q0n	D3	D2	D1	D0	Q3n+1	Q2n+1	Q1n+1	Q0n+1	J3	K3	J2	K2	J1	K1	J0	K0	D3	D2	D1	D0	L	UP
0	0	0	0	0	0	0	x	x	0	0	x	x	1	0	x	0	x	1	x	x	0	0	1	1	1	x
1	0	0	0	0	1	0	0	0	1	0	0	x	x	x	0	x	x	x	x	x	x	x	x	x	x	x
2	0	0	0	1	0	0	1	0	1	0	0	x	x	x	0	x	1	x	x	x	x	x	x	x	x	x
3	0	0	1	0	1	0	0	0	1	0	0	x	x	x	0	x	0	x	1	x	x	x	x	x	x	x
4	0	0	1	1	0	0	0	0	1	0	0	x	x	x	0	x	0	x	0	x	x	x	x	x	x	x
5	0	0	1	0	1	0	0	0	1	0	0	x	x	x	1	0	x	x	0	1	x	x	x	x	x	x
6	0	1	1	1	0	0	x	x	x	0	0	x	x	x	0	x	x	0	x	x	x	x	x	x	x	x
7	0	0	1	1	1	0	0	1	0	0	0	x	x	x	0	x	x	0	1	0	0	1	x	x	x	x
8	1	0	0	0	0	0	x	x	x	0	0	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x
9	1	0	0	0	0	1	x	x	x	0	0	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x
10	1	0	0	1	0	0	1	1	1	1	1	x	x	x	1	x	0	1	x	x	x	x	x	x	x	x
11	1	0	0	1	1	0	1	0	1	1	1	x	x	x	1	x	1	1	1	1	1	1	1	1	1	1
12	1	1	0	0	0	0	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x
13	1	1	0	0	1	0	1	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x
14	1	1	1	1	0	0	0	0	0	0	0	x	x	x	0	x	1	x	1	0	x	0	0	0	0	1
15	1	1	1	1	1	1	1	1	1	1	1	0	x	x	x	0	x	0	x	1	1	1	0	0	0	0


$$J_3 = K_3 = Q2 * \overline{Q0}$$





Inputs		Outputs											
CLR	L	CE	C	UP	Dz-D0	Qz-Q0	TC	CEO	D3 D2 D1 D0 L UP				
1	X	X	X	X	X	0	0	0	0	0	1	1	1
0	1	X	1	X	Dn	Dn	TC	CEO	0	0	1	1	1
0	0	0	X	X	No change	No change	0	0	1	1	1	1	1
0	0	1	1	1	X	Jnc	TC	CEO	x	x	x	x	x
0	0	1	1	1	0	Dec	TC	CEO	x	x	x	x	x
0	0	1	1	1	0	X	Dec	CEO	x	x	x	x	x

z = bit width - 1
TC = $(Qz \oplus Q(z-1)) \oplus Q(z-2) \oplus \dots \oplus Q(0) \oplus P$ + $(Qz \oplus Q(z-1)) \oplus Q(z-2) \oplus \dots \oplus Q(0) \oplus P$
CEO = TC \oplus CE


$$J_2 = Q1 * \overline{Q0}$$

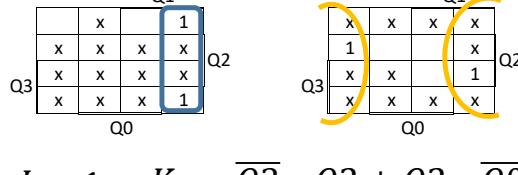
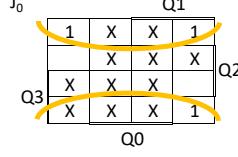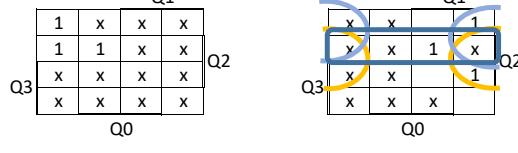
$$J_1 = 1 \quad K_1 = \overline{Q3} * Q2 + Q2 * \overline{Q0} + \overline{Q3} * \overline{Q0}$$



$$J_0 = \overline{Q2}$$

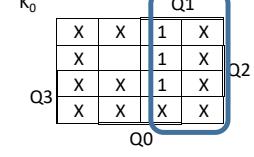

$$K_0 = Q1$$